

Digital Logic: Project 2 Block Diagrams

Anderson, Anna `anna.anderson@colorado.edu`

Cuthbertson, Sam `samuel.cuthbertson@colorado.edu`

April 30, 2017


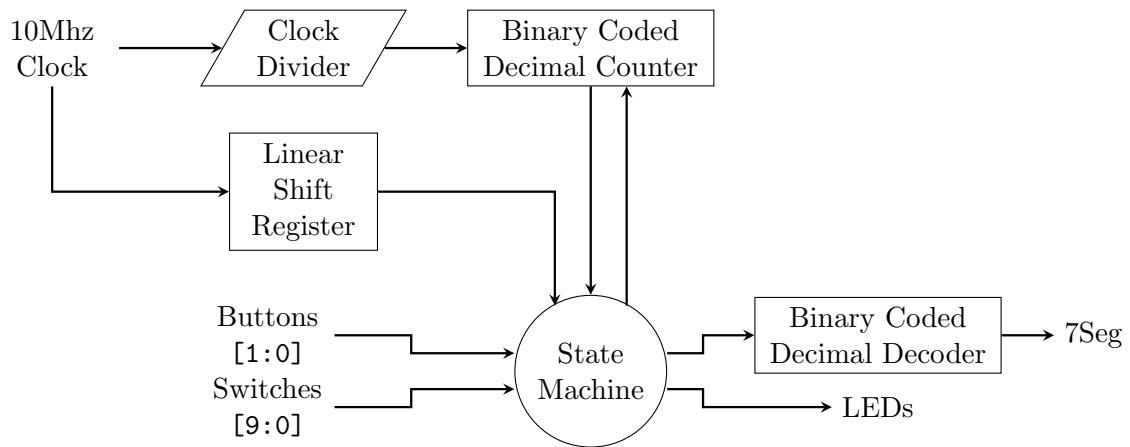


Figure 1: Our block diagram for top.v.

 

State Name	Description
PS	Mode we boot into, displays highscore.
GB	Displays a scrolling "Go Buffs".
RW	Waits a random time interval.
UW	Counts the time spent here.
DS	Displays the value from the counter, updates highscore.

Figure 2: Our graph for the State Machine in top.v, where B0 is the start button, B1 is the reset button, and SW is assumed to be the correct switch. Additionally, all buttons are assumed to be active-low and all switches are assumed to be active-high.