


1. *Book Problems: 5.7, 5.10, 5.16, 5.25*

5.7: *Show how a JK flip-flop can be implemented with a T flip-flop and other gates.*

Note that the characteristic equations for a T flip-flop and for a JK flip-flop are both shown below.

T	$Q(t+1)$	J	K	$Q(t+1)$
0	$Q(t)$	0	0	$Q(t)$
1	$\overline{Q(t)}$	0	1	0
		1	0	1
		1	1	$\overline{Q(t)}$

 Therefore, for $J = K$ or $J \otimes K$, we can use J as T. For $J \neq K$, we need to set $T = J \oplus Q(t)$, as that will set $T = 1$ when $Q(t) \neq J$ and will toggle $Q(t+1)$. This is implemented below.



5.10: *Write the behavioral Verilog code for a JK flip-flop.*


```

module jk_flip_flop(J, K, CLK, Q, nQ)
    input reg J, K, CLK;
    output reg Q, nQ;

    always@(posedge CLK)
    begin
        case({J, K})
            {1'b0, 1'b1}: Q <= 1'b0;
            {1'b1, 1'b0}: Q <= 1'b1;
            {1'b1, 1'b1}: Q <= ~Q;
        endcase
        nQ = ~Q
    end
endmodule
    
```

 5.16: Design a three bit up/down counter using D flip-flops, using a control signal of $\overline{UP}/DOWN$.

For an up counter, we can use the equations $D_0 = Q_0 \oplus 1$, $D_1 = Q_1 \oplus Q_0$, $D_2 = Q_2 \oplus Q_1Q_0$. For a down counter, the equations are similar: $D_0 = Q_0 \oplus 1$, $D_1 = \overline{Q_0} \oplus Q_1$, $D_2 = \overline{Q_1} \oplus Q_1Q_2$. As the only difference between these is whether to use Q_{n-1} or $\overline{Q_{n-1}}$ in the xor with the previous and, we can use a mux at each stage with our control signal as a select.



5.25: Using the circuit shown in the book, complete the below timing diagram.

Placeholder answer

2. *Draw a 4-bit Universal shift register that can parallel load, shift left, shift right, and synchronously clear. Provide a characteristic table for the control operations.*

Placeholder answer

3. *Implement a 3-bit up-counter using only one D flip-flop, one T flip-flop, one JK flip-flop and one AND gate. Assume all flip-flops are positive edge triggered. Show your circuit and a timing diagram.*


You don't have a power source or a clock, so all of this is moot, but if you could find both of those then you could implement an up counter as shown below.

As the first bit Q_0 changes with every posedge of clock, we can simply attach $\overline{Q_0}$ to the input of the D and use that output for Q_0 .

Similarly, as Q_1 toggles between 1 and 0 every time $\overline{Q_0}$ changes from 0 to 1 (posedge) we can attach 1 as the input to the T flip-flop and $\overline{Q_0}$ to the clock, and then use the output from the T flip-flop as Q_1 .

Finally, as Q_2 toggles everytime that $\overline{Q_0Q_1}$ goes 0 to 1 (posedge), we can attach the output from that **and** gate to both J and K, making the JK flip-flop behave like a T flip-flop. Then, we can use the output from the JK flip-flop as Q_2 .

All this put together is shown below:

 

4. Write the behavioural Verilog for 5.16, calling the module *up_down_counter*.

```
module up_down_counter(clk, ctrl, value);
    input clk;
    input ctrl;
    output reg [2:0] value;

    always@(posedge clk)
    begin
        case(ctrl)
            1'b0: value <= value - 1;
            1'b1: value <= value + 1;
        endcase
    end
endmodule
```