
1. *Book Problems: 4.3, 4.21*

(4.3) *Consider $f = \overline{w_1}\overline{w_3} + w_2\overline{w_3} + \overline{w_1}w_2$. Use the truth table to derive a circuit for f that uses a 2-to-1 multiplexer.*

ASDDSD

(4.21) *Write Verilog code for an 8-to-3 binary encoder.*

WOW

2. *Implement the following circuits using only 2-to-1 multiplexers.*

(a) $f = \sum m(2, 5, 6, 14)$

Wow look

(b) $f = \prod M(3, 4, 5, 6, 7)$

Golly gee

3. *Convert the following decimal numbers to 32-bit floating point format.*

(a) *33554430*

Hey ho

(b) *33554431*

Let's go

4. *Convert the following decimal numbers to fixed point unsigned binary with at least 8-bits of binary precision*

(a) *12.45897*

What now

(b) *0.333333*

To much placeholdering

5. *For 32-bit Precision Floating point numbers, $E=0x00$ and $E=0xFF$ are used for special numbers (like 0 and ∞). What are the decimal values of the floating point numbers (32-bit) of smallest (non-zero) and largest (non-infinity) magnitude*